

# KEY

## ECE 273 Final Exam

04.29.02

Version B

Name:

Honor Code:


### Instructions:

- As discussed in class, there are 5 problem categories resulting in 6 problems:
  - (15%) Complete state machine design (problem 5)
  - (19%) State assignment, minimization, and realization (problem 6)
  - (18%) Multiple-input / Multiple-output devices. (problem 1)
  - (25%) Various short minimization problems (problem 2)
  - (23%) Short problems for misc. topics (problem 3 and problem 4)
- Work the problems in the space provided. Do not use a bluebook. If you need additional paper, put your name on it and attach it to the exam.
- Make sure the location of your answers is clear (circle them if necessary).
- Each problem has a set number of points assigned to it, designated by a number in square brackets. Problems with subparts have the point value for each subpart similarly marked.
- If you're not sure about something, *ask*. I will be happy to clarify, reword, or explain the intent of a question to you and the class. Someone else is probably wondering the same thing.
- Don't panic.

[18] 1. Complete the following problems dealing with multiple-input / multiple-output devices

[10] (a) Show how to implement the following logic table using a ROM.


	Input			Output			
	A	B	C	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
2	0	1	0	0	1	1	1
3	0	1	1	0	1	0	1
4	1	0	0	1	1	0	0
5	1	0	1	0	0	0	1
6	1	1	0	1	1	1	1
7	1	1	1	0	1	0	1

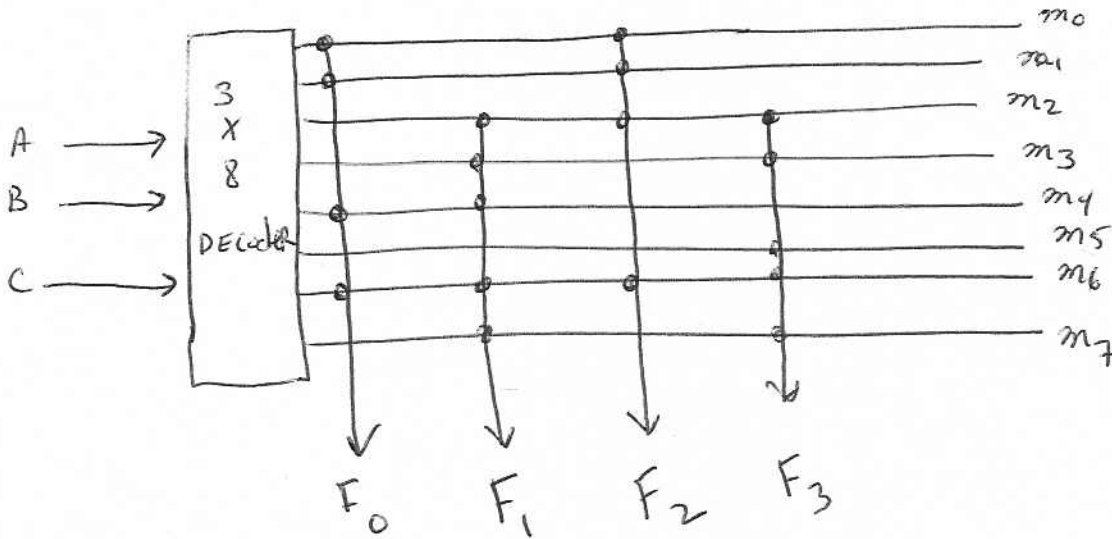

✓

[4] (b) Show how to use a 3-8 Line Decoder to implement  $f(a,b,c) = ab + a'c'$

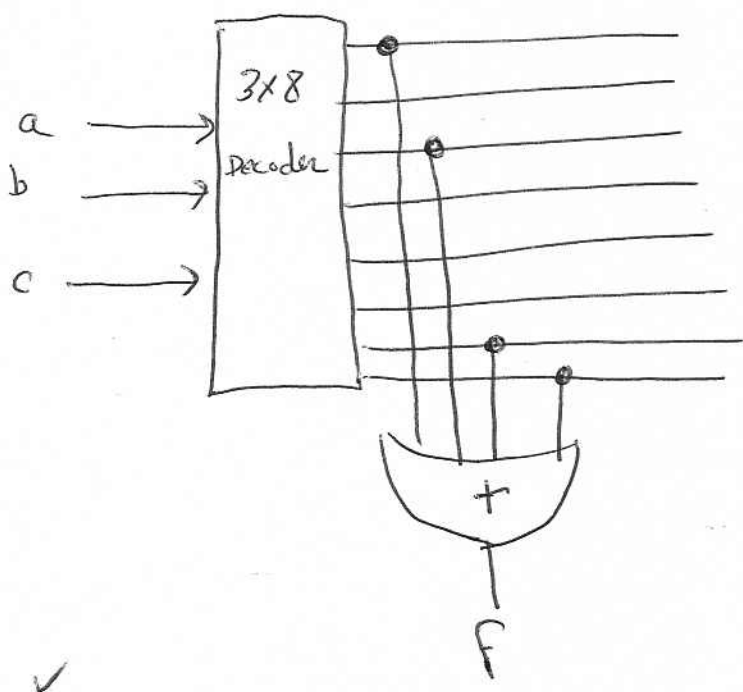
$$\begin{aligned}
 &= abc + abc' \\
 &\quad + a'bc' + a'b'c' \\
 &= \sum m(0, 2, 6, 7)
 \end{aligned}$$



✓

[4] (c) Show how to implement  $f(a,b,c) = ab + a'c'$  using a 4x1 multiplexer.
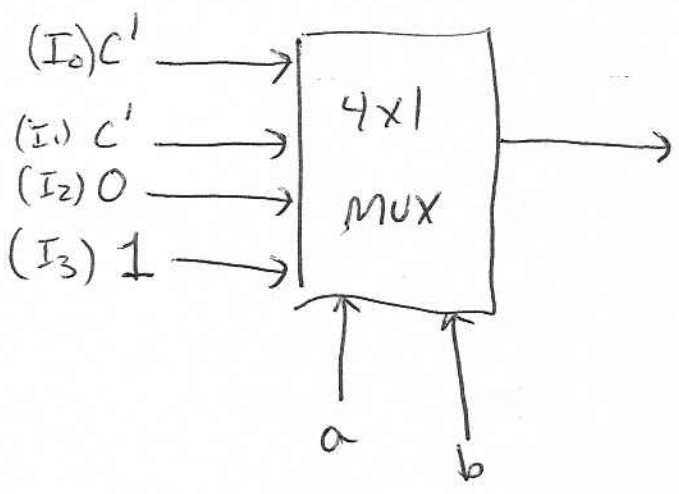
$$\begin{aligned}
 &= abc + abc' + a'bc' + a'b'c' \\
 &= ab(c + c') + a'b(c') + a'b'(c') \\
 &\quad + ab'(0) + \dots
 \end{aligned}$$



[25] 2. Simplify each of the following as directed [2.5 points each]. Write your answers next to the question and use the following pages for your work.

Simplify to *minimum sum of products* form.

(a)  $(A + B + C)(A' + B' + D')(A' + B' + C')(A + B + D)$

(b)  $(A' + B + D)(A + C)(A + B' + D)(A' + C' + D')(A' + B)$

(c)  $f(a, b, c, d) = \sum m(1, 3, 5, 7, 9, 12)$

(d)  $f(a, b, c, d) = \prod M(0, 2, 4, 6, 8, 10, 11)$

Write in *product of sums* form (doesn't need to be minimum POS form)

(e)  $ab + a'c' + a'bc$

(f)  $a'b'c' + abd + a'c + a'cd' + ac'd + ab'c'$

Write in *minterm* form (i.e. write as  $f = \sum m(\dots)$ )

(g)  $f(a, b, c, d) = (abc'd + abcd + a'b'c'd' + abcd' + ab'c'd + ab'c'd' + a'bcd + a'b'cd)'$

(h)  $f(a, b, c, d) = ab + c'd$

Write in *maxterm* form (i.e. write as  $f = \prod M(\dots)$ )

(i)  $f(a, b, c, d) = [(a + b + c + d)(a' + b' + c + d')(a + b' + c' + d)(a + b + c' + d)(a' + b + c' + d)]'$

(j)  $f(a, b, c, d) = (a + b)(c' + d)$

✓ (a)  $(a+b+c)(a'+b'+c')(a'+b'+d')(a+b+d)$

$ab' + ac' + a'b + bc' + a'c + b'c$

$(a+b+c)(a+b+d)(a'+b'+d')(a'+b'+c')$

$\{(x+y)(x+z) = x+yz\}$

$= (a+b+cd)(a'+b'+c'd') = ab' + ac'd' + a'b + bc'd' + a'cd + b'cd$

	ab	00	01	11	10
cd	00	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$\rightarrow a'b + ab' + a'cd + ac'd'$

$$(b) \underbrace{(a'+b+d)(a'+b)}_{(a'+b)} \underbrace{(a+c)(a+b'+d)(a'+c'+d')}_{(a+c)(ac'+ad'+a'b'+b'c'+b'd'+a'd+c'd')}$$

$$(a'c + ab + bc)(ac'+ad'+a'b'+b'c'+b'd'+a'd+c'd)$$

$$= (a'b'c + a'b'cd' + a'b'cd + a'cd + abc' + abd' + abe'd + abcd' + a'bcd)$$

		ab			
cd	00	01	11	10	
00			1		
01			1		
11	1	1		1	
10	1		1		

$$= abc' + a'cd + a'b'c + abed' + a'b'cd$$

✓ (c)

		ab			
cd	00	01	11	10	
00			1		
01	1	1		1	
11	1	1			
10					

$$= a'd + abc'd + abc'd'$$

✓ (d)  $f(a,b,c,d) = \sum m(1,3,5,7,9,12,13,14,15)$

		ab			
cd	00	01	11	10	
00			1		
01	1	1	1	1	
11	1	1	1		
10				1	

$$= ab + c'd + a'd$$

✓(e)

		a	
	b	0	1
c	00	1	0
	01	0	0
	11	1	1
	10	1	1

$$f' = ab' + b'c$$

$$f = (a'+b)(b+c')$$

(f)

		cd			
	ab	00	01	11	10
c	00	1	0	0	0
	01	1	1	1	1
	11	1	1	1	0
	10	1	1	0	0

$$f = (b'+c+d)(a'+b+c')$$

$$(a'+c'+d)$$

✓

$$(g) f = [\sum m(13, 15, 0, 14, 6, 8, 7, 2)]' = \sum m(1, 3, 4, 5, 9, 10, 11, 12)$$

✓

$$(h) f = ab + c'd$$

$$11xx \quad xx01$$

$$= \sum m(12, 13, 14, 15, \bar{1}, \bar{5}, \bar{9}, 13) = \sum m(1, 5, 9, 12, 13, 14, 15)$$

✓

$$(i) f = (\prod M(0, 13, 6, 2, 10))' = \prod M(1, 3, 4, 5, 7, 8, 9, 11, 12, 14, 15)$$

✓

$$(j) f = (a+b)(c'+d) = ac' + ad + bc' + bd$$

		cd			
	ab	00	01	11	10
c	00	0	1	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	0	0	0

$$f' = a'b' + cd'$$


$$f = (a+b)(c'+d)$$

$$= \prod M(0, 1, 2, 3, 4, 6, 10, 14)$$

$$= \sum m(5, 7, 8, 9, 11, 12, 13, 15)$$

[15] 3. Work the following short problems

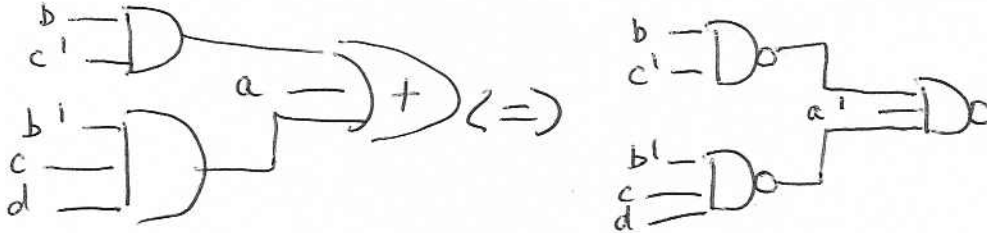[3] (a) Draw a circuit diagram for  $f = a + bc' + b'cd$  using only NAND gates.




[3] (c) Given  $f(a,b,c) = \sum m(0,1,2,3,6,7)$ , find the minimum SOP form using the QM method.

Level I	Level II	Level II
✓ 0 000	✓ (0,1) 00-	(0,1,2,3) 0--
✓ 1 001	✓ (0,2) 0-0	<del>(0,2,1,3) 0</del>
✓ 2 010	✓ (1,3) 0-1	(2,6,3,7) -1-
✓ 6 110	✓ (2,6) -10	<del>(2,3,6,7) -</del>
✓ 3 011	✓ (2,3) 0+-	
	✓ (6,7) 11-	
✓ 7 111	(3,7) -11	


$\underline{a' + b}$

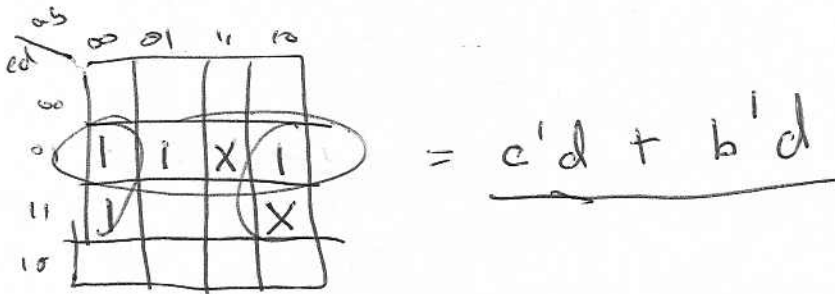[3] (d) Find a minimum SOP for  $f(a,b,c,d) = \sum m(1,3,5,9) + \sum d(11,13)$




✓

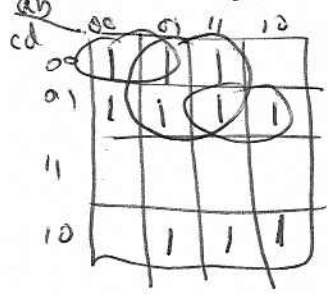[3] (e) Draw  $f(a,b,c,d) = \sum m(1,5,6,10,13,14)$  using 3 OR gates and 2 AND gates by factoring.



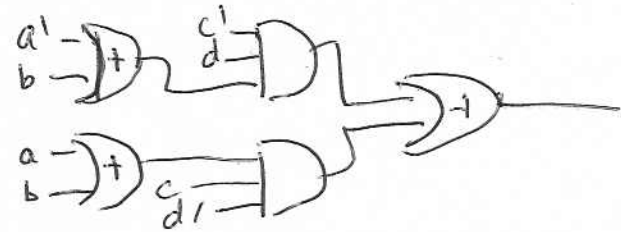
$$\begin{aligned}
 &= a'c'd + bc'd \\
 &= \cancel{a'c'd} + bc' + \cancel{ac'd} + bcd' + acd' \\
 &= \cancel{c'(a'd' + b + ad)} = c'd(a'+b) + cd'(a+b)
 \end{aligned}$$



✓

(Clock)

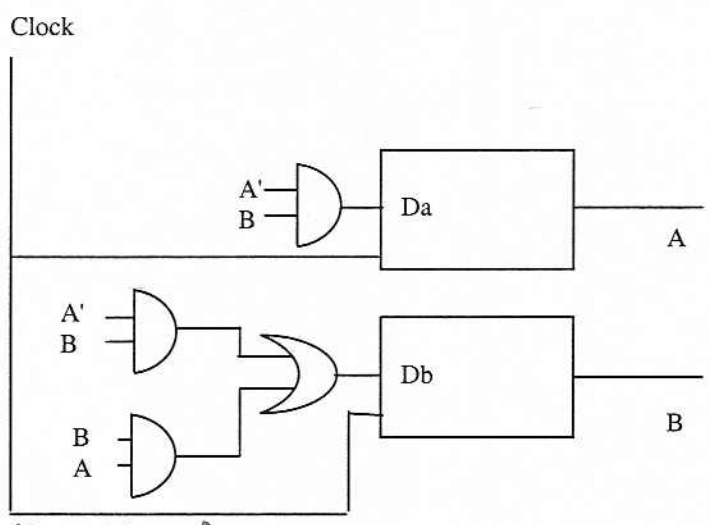[3] (f) Given the input sequence  $X=011$  and the initial state  $AB=00$ , write the output sequence  $A$  for the circuit below.




State 00 00 00  
 $A = 0 0 0$




[8] 4. Answer True or False [2 points each]. Write your answers next to the question; use the bottom of this page for your work.

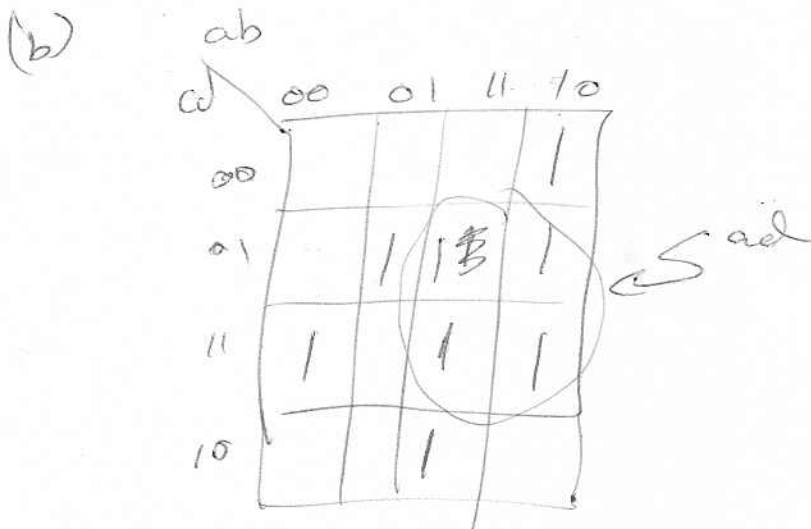- T ✓ (a) An 8-1 MUX can implement any function of 3 variables.
- F ✓ (b)  $abc + ab'c' + b'cd + bc'd + ad = abc + ab'c' + b'cd + bc'd$
- F ✓ (c)  $(x+y)(y+z)(x+z) = (x+y')(y'+z')(x'+z')$
- F ✓ (d) If  $f_1(a,b,c,d) = \sum m(1,3,5,7)$  and  $f_2(a,b,c) = \sum m(1,3,5,7)$  then  $f_1 = f_2$




[15] 5. Design the following state machines. You need only draw a state graph and state table that meets the description.

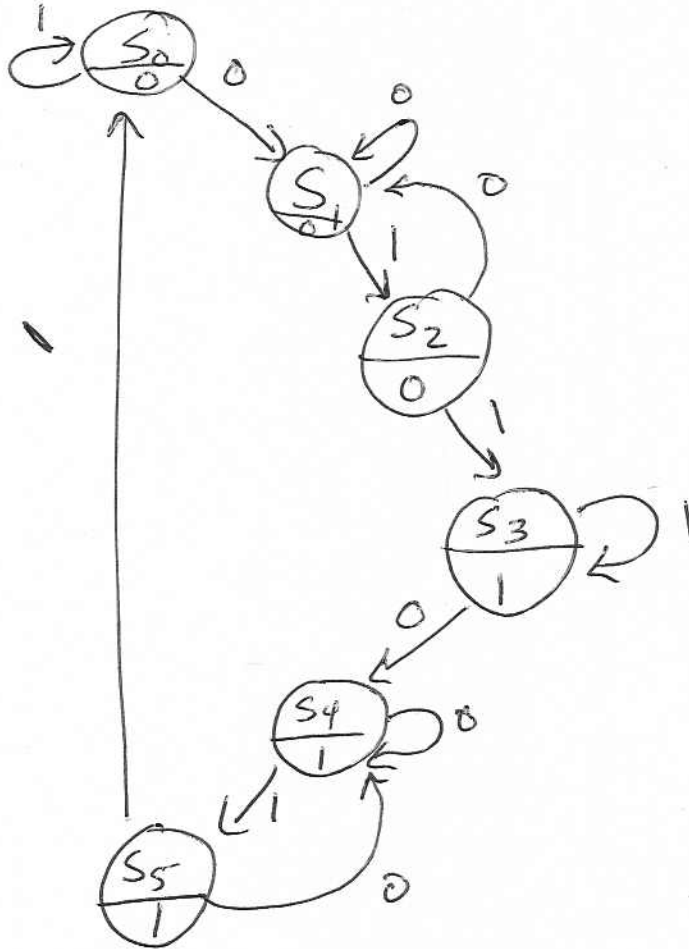[7] (a) Design a Moore machine that has one output bit ( $Z$ ) and one input bit ( $X$ ). When the input sequence 011 occurs, the output becomes 1 and remains 1 until 011 occurs again; at which time the output returns to 0. The output remains 0 until 011 is detected again, etc. You should be able to design this with 6 states.



	next		output
$S_0$	$S_1$	$S_0$	0
$S_1$	$S_1$	$S_2$	0
$S_2$	$S_1$	$S_3$	0
$S_3$	$S_4$	$S_3$	1
$S_4$	$S_4$	$S_5$	1
$S_5$	$S_4$	$S_0$	1

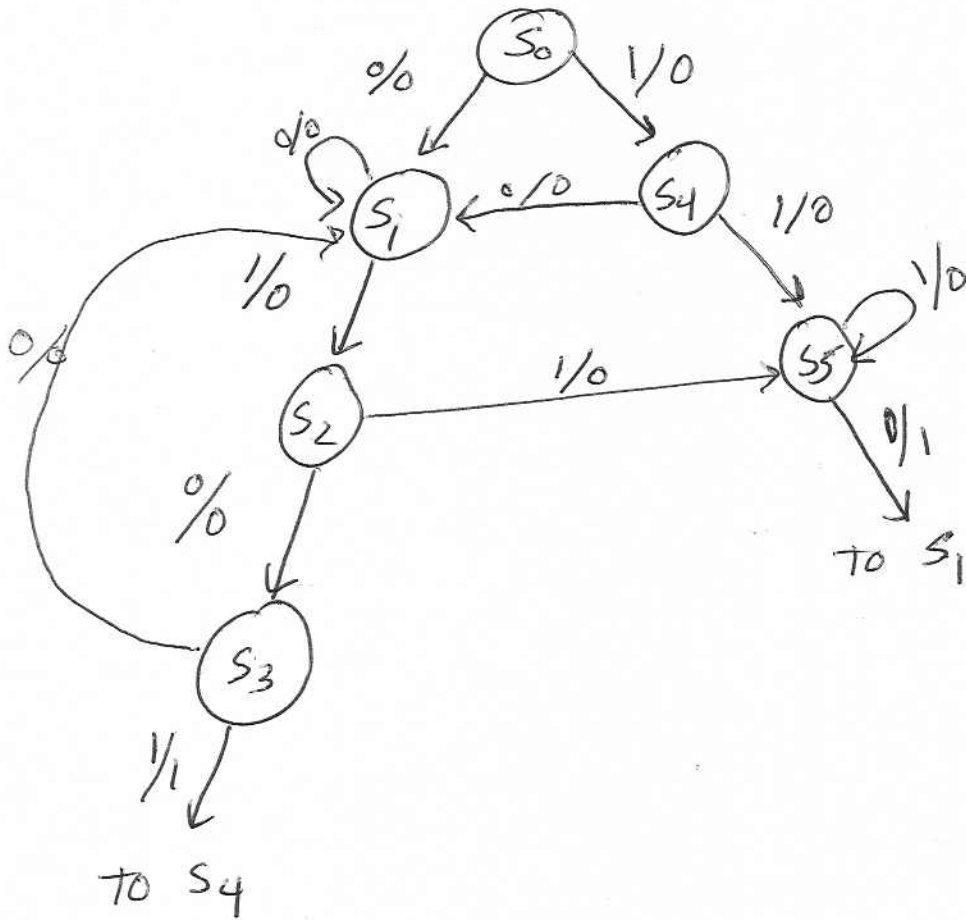[8] (b) Design a Mealy machine that detects the sequences 0101 and 110 simultaneously.




	next		output	
S <sub>0</sub>	S <sub>0</sub>	S <sub>4</sub>	0	0
S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
S <sub>2</sub>	S <sub>3</sub>	S <sub>5</sub>	0	0
S <sub>3</sub>	S <sub>1</sub>	S <sub>4</sub>	0	1
S <sub>4</sub>	S <sub>1</sub>	S <sub>5</sub>	0	0
S <sub>5</sub>	S <sub>1</sub>	S <sub>5</sub>	1	0

[19] 6. Given the state table

Present State	Next State				Output			
	X=00	X=01	X=10	X=11	X=00	X=01	X=10	X=11
a	a	a	g	ki	1	0	0	0
b	c	f	g	da	0	0	0	0
c	g	c	a	i	1	0	0	0
<del>d</del>	<del>a</del>	<del>d</del>	<del>g</del>	<del>i</del>	<del>1</del>	<del>0</del>	<del>0</del>	<del>0</del>
e	f	hc	g	a	0	0	0	0
f	da	c	da	ki	1	0	0	0
g	c	i	g	e	0	1	0	0
<del>h</del>	<del>g</del>	<del>h</del>	<del>da</del>	<del>ki</del>	<del>1</del>	<del>0</del>	<del>0</del>	<del>0</del>
i	hc	dc	g	da	0	0	0	0
<del>j</del>	<del>j</del>	<del>j</del>	<del>g</del>	<del>k</del>	<del>1</del>	<del>0</del>	<del>0</del>	<del>0</del>
<del>k</del>	<del>e</del>	<del>e</del>	<del>g</del>	<del>d</del>	<del>0</del>	<del>0</del>	<del>0</del>	<del>0</del>

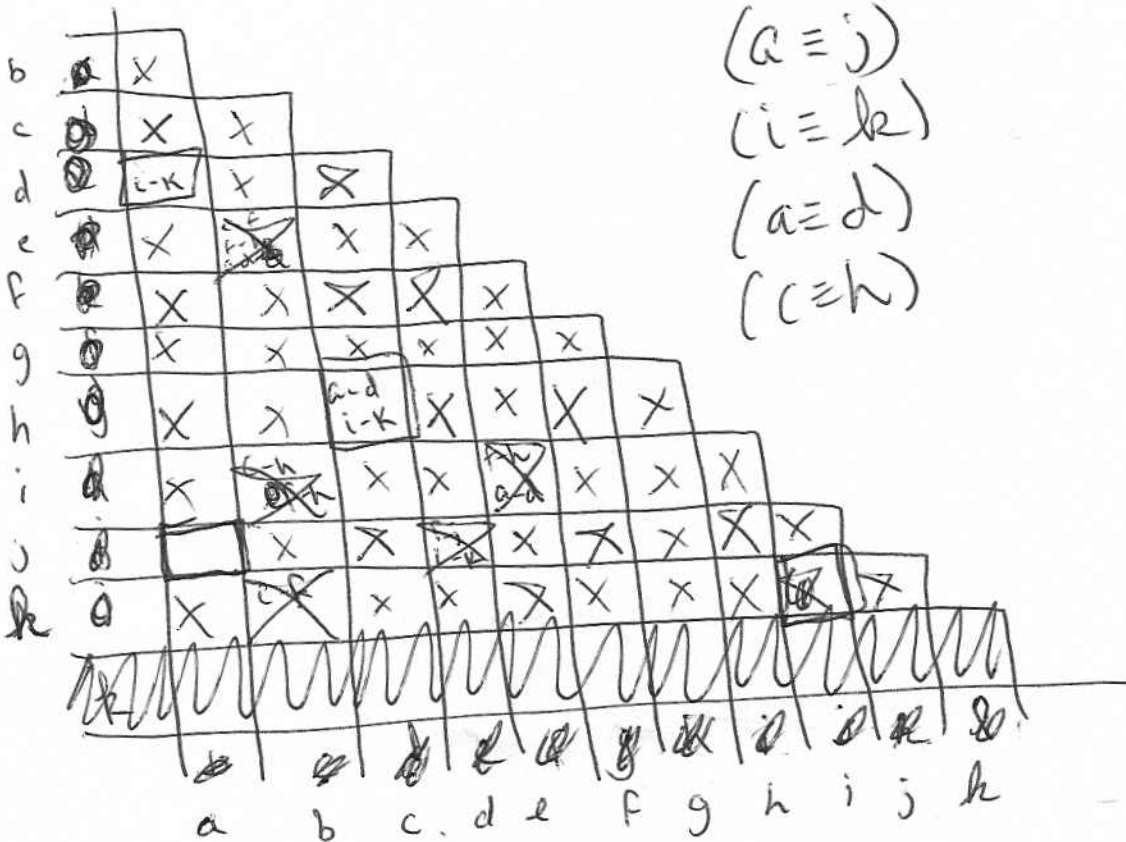[9] (a) Find the minimum number of states and write the minimal state table.



[6] (b) Find a 'good' assignment of flip-flop outputs to states and explain your work.

[4] (c) Draw the circuit resulting from this assignment.